

TYPES OF ROM:

- Mask ROM.
 - Programmable ROM(PROM).
 - Erasable ROM(EROM).
 - Ultraviolet EPROM(UV PROM).
 - Electrically Erasable PROM(EEPROM)
-
- Assignment: Discuss each type of ROM in brief.

Programmable Array Logic(PAL):

- PAL is programmable array of logic gates on a single chip.
- The basic PAL consists of a programmable AND array and fixed OR array with output logic as shown in block diagram below.
- PAL is most common one time programmable(OTP) Logic device and is implemented with bipolar technology(TTL or ECL)

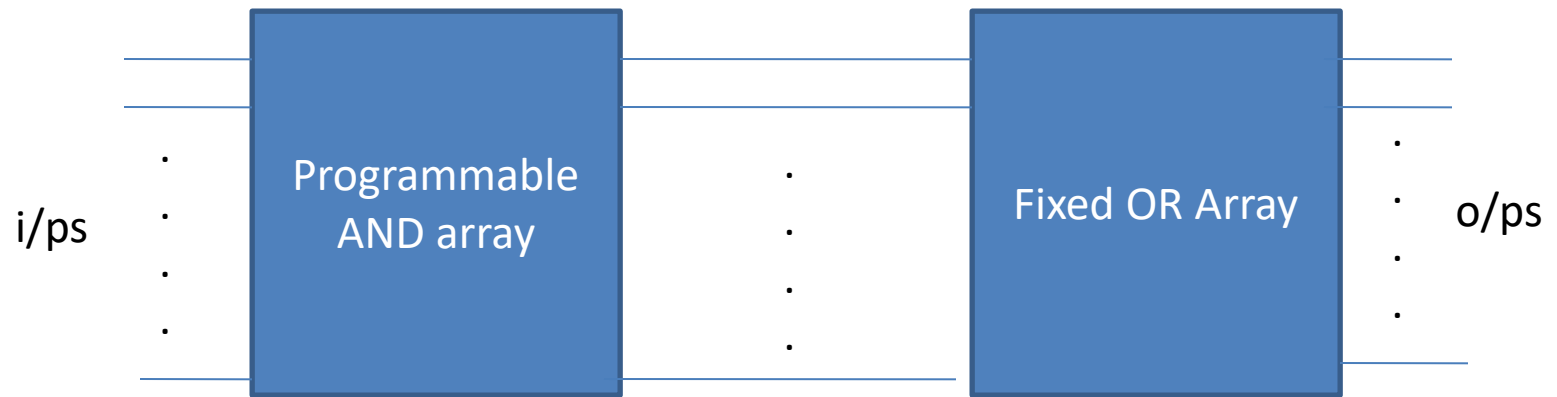


Fig: Block diagram of PAL

Programmable Logic Array:

- A PLA consists of a programmable AND array and a programmable OR array.
- The PLA is also called a field programmable Logic array (FPLA) because the user in the field programs it, not the manufacturer.
- The use of PLA must be considered for combinational circuits that have a large number of input and outputs. It is superior to a ROM for circuits that have a large

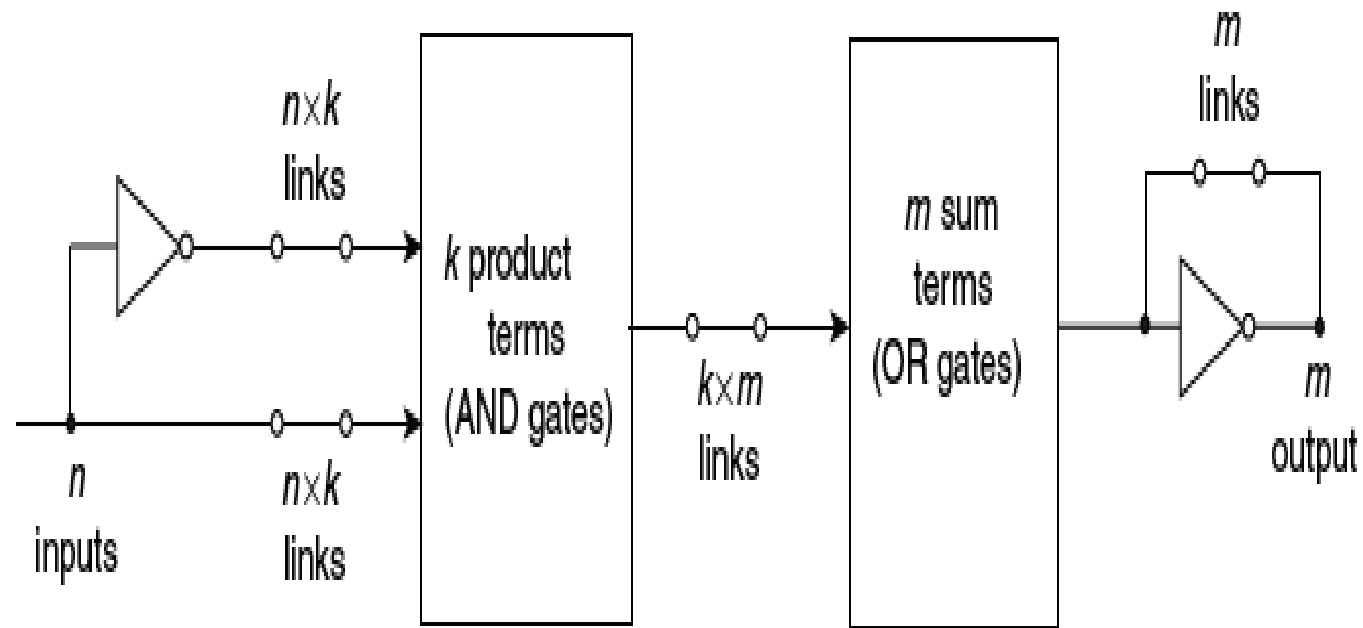


Figure 5-25 PLA block diagram


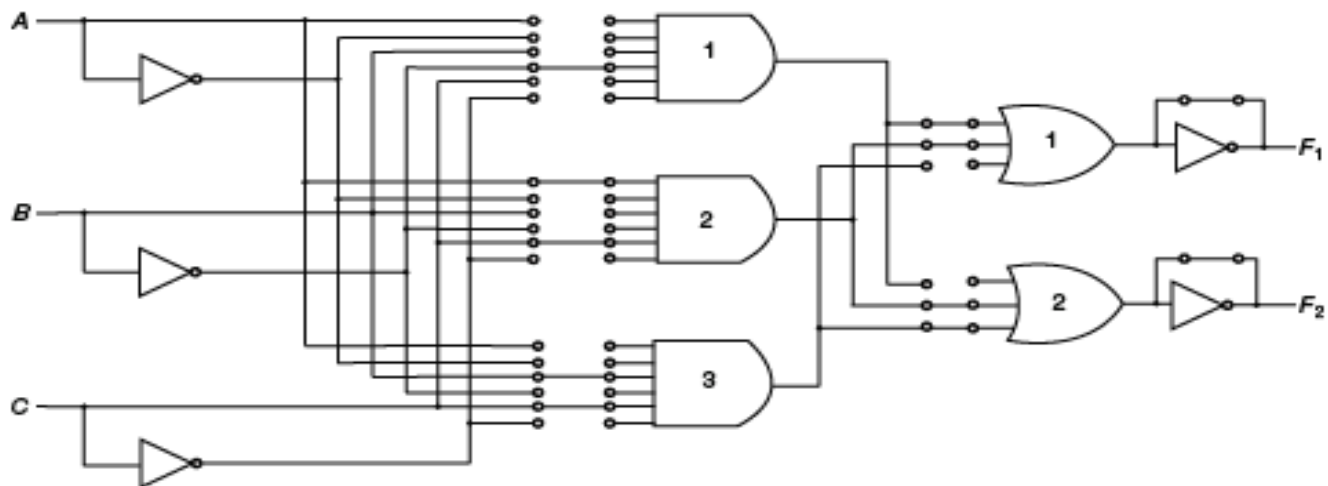


Figure 5-26 PLA with 3 inputs, 3 product terms, and 2 outputs; it implements the combinational circuit specified in Fig. 5-27

Implement function using PLA

- $F0 = \text{sm}(0,1,4,6)$
- $F1 = \text{sm}(2,3,4,6,7)$
- $F2 = \text{sm}(0,1,2,6)$

$$Y = \overline{A}B + \overline{A}C$$

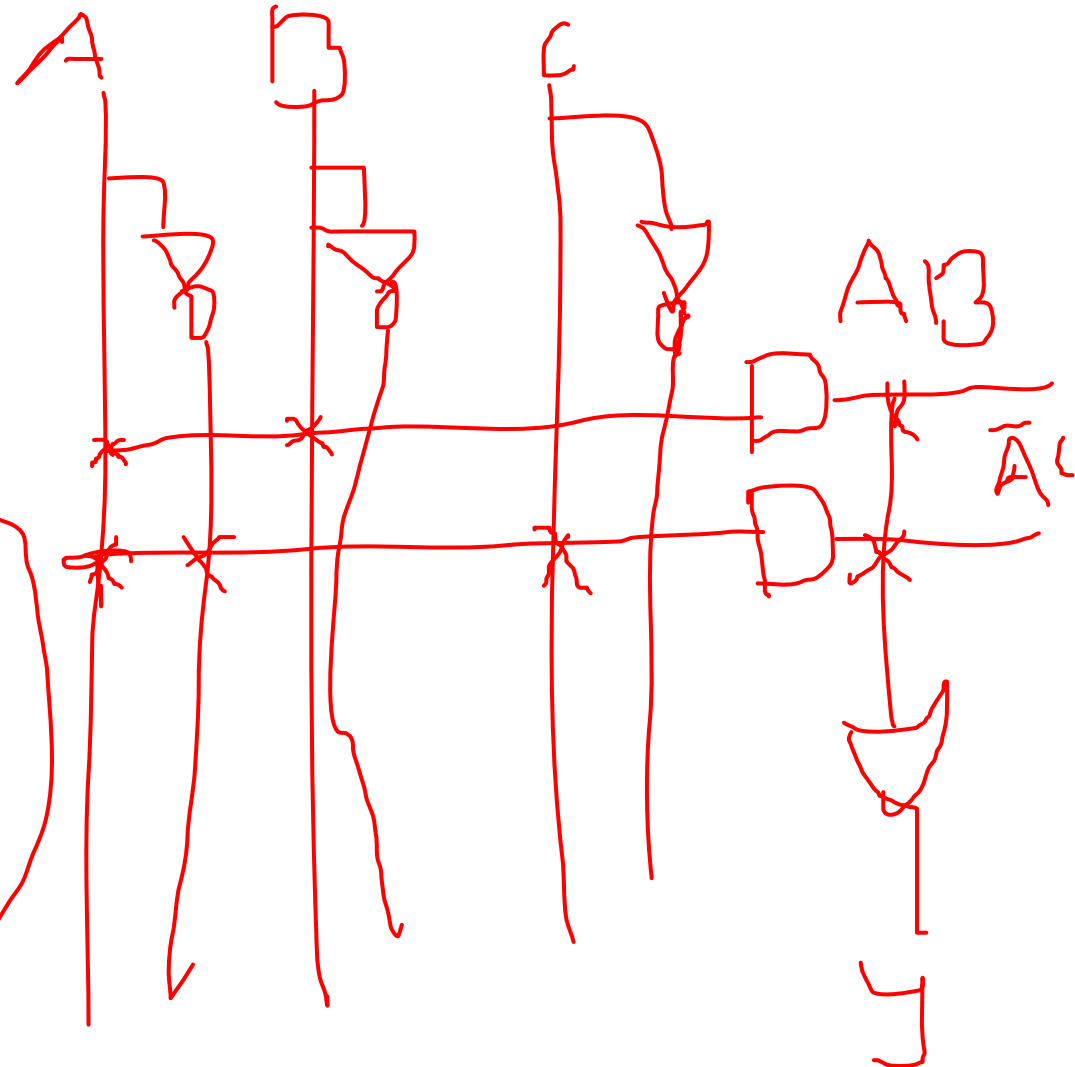

EXAMPLE 5-6: A combinational circuit is defined by the functions:

$$F_1(A, B, C) = \Sigma(3, 5, 6, 7)$$


$$F_2(A, B, C) = \Sigma(0, 2, 4, 7)$$

Implement the circuit with a PLA having three inputs, four product terms, and two outputs. The two functions are simplified in the maps of Fig. 5-28. Both the true values and the complements of the functions are simplified. The combinations that gives a minimum number of product terms are:

$$F_1 = (B'C + A'C' + A'B')'$$

$$F_2 = B'C + A'C' + ABC$$

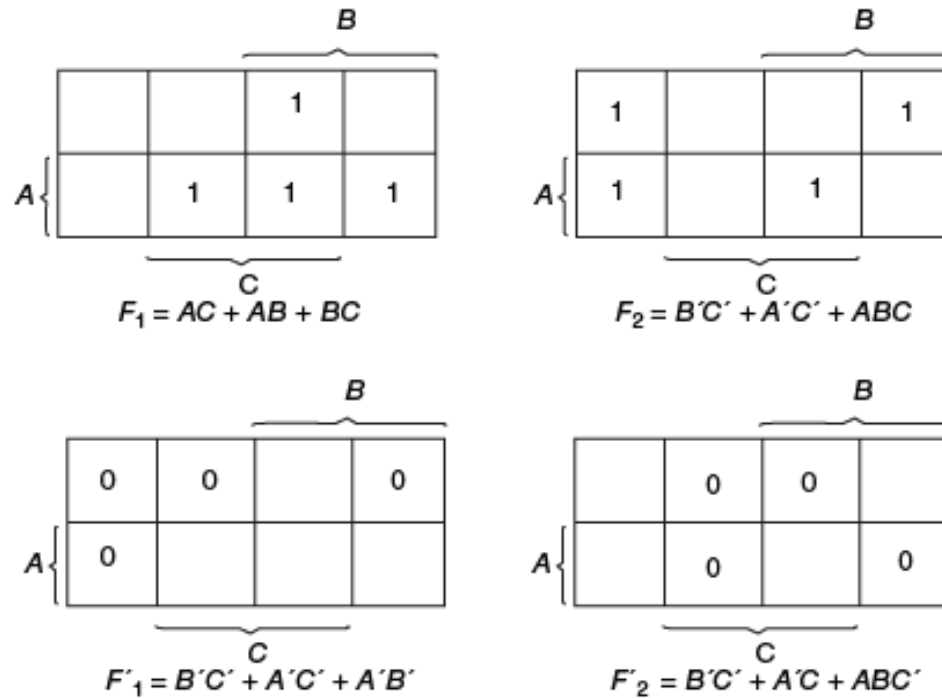This gives only four distinct product terms: $B'C$, $A'C'$, $A'B'$, and ABC . The PLA program table for this combination is shown in Fig. 5-28. Note that output F_1 is the normal (or true) output even though a C is marked under it. This is because F_1' is generated *prior to* the output inverter. The inverter complements the function to produce F_1 in the output.



PLA program table

	Product term	Inputs			Outputs	
		A	B	C	F_1	F_2
$B'C'$	1	-	0	0	1	1
$A'C'$	2	0	-	0	1	1
$A'B'$	3	0	0	-	1	-
ABC	4	1	1	1	-	1
					C	T
					T/C	

Figure 5-28 Solution to Example 5-6

Implement a full adder using PLA:

- Output= sum and carry
- Sum= $\text{sm}(1,2,4,7) = A'B'C + A'BC' + ABC + AB'C'$
- Carry= $\text{sm}(3,5,6,7) = A'BC + AB'C + ABC' + ABC$